Circuit Diagram for Smart Blind Stick

Ultrasonic Sensor

Buzzer

Breadboard

LED

R 220Ω

Arduino UNO